

Q-1: Draw the circuit of Fig 1 in your answer script and mark down all the nodes.



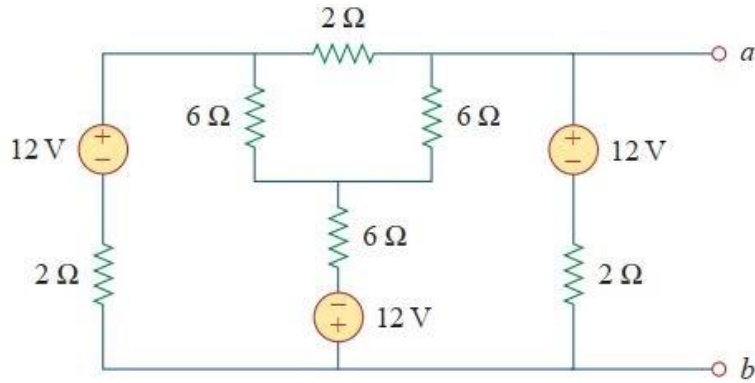


Fig 1

Ans:

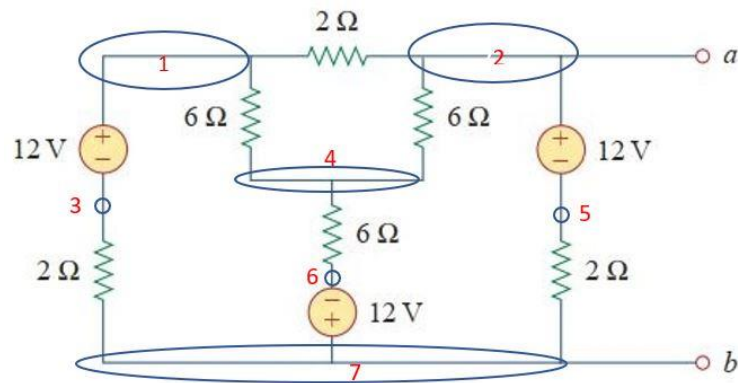

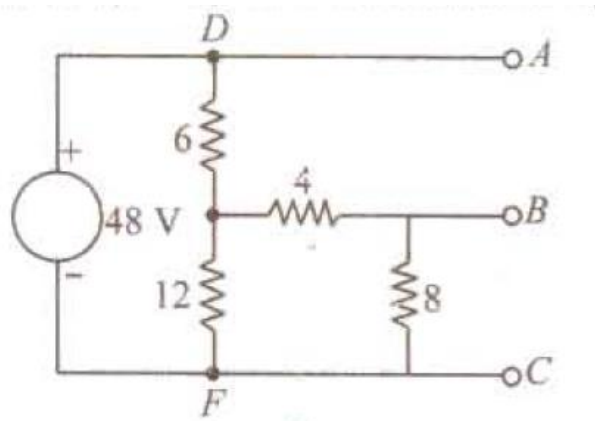Q-2: Calculate the value of V_{th} and R_{th} between terminals B and C of the circuit shown in Fig 2. All resistance values are in ohms.



Ans:


V_{th}:

$$R_{EF} = 12 \parallel (4+8) = 6\Omega$$

$$V_{EF} = 48 \times \frac{6}{6+6} = 24\text{ V}$$

$$V_{BC} = 24 \times \frac{8}{4+8} = 16\text{ V (Ans)}$$

R_{th}:

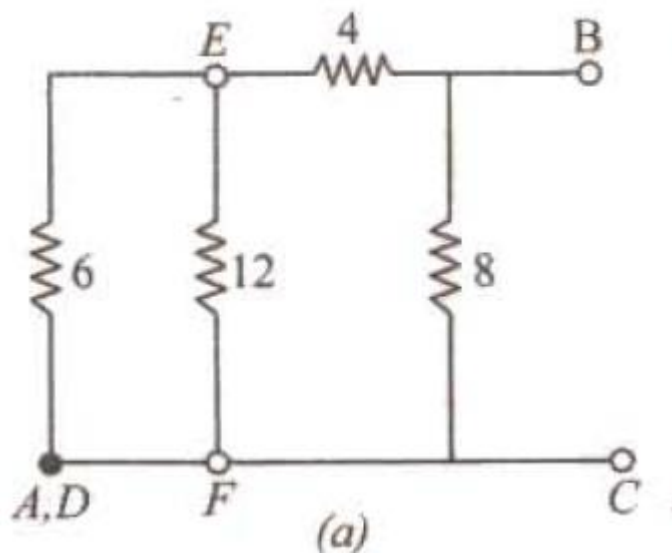

$$R_{th} = ((6 \parallel 12) + 4) \parallel 8 = 4\Omega \text{ (Ans)}$$

Q-3: Calculate V_0 of the following circuit (Fig 3) using nodal analysis.


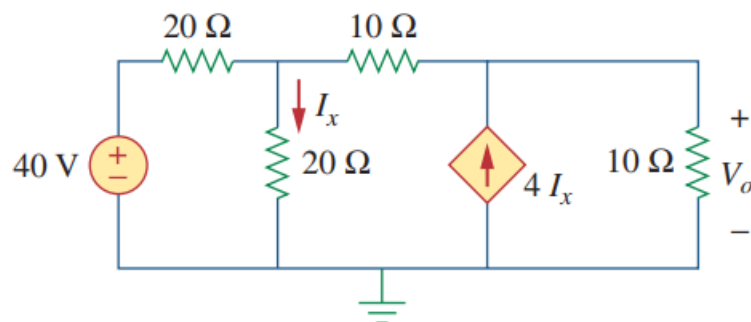


Fig 3

Ans:

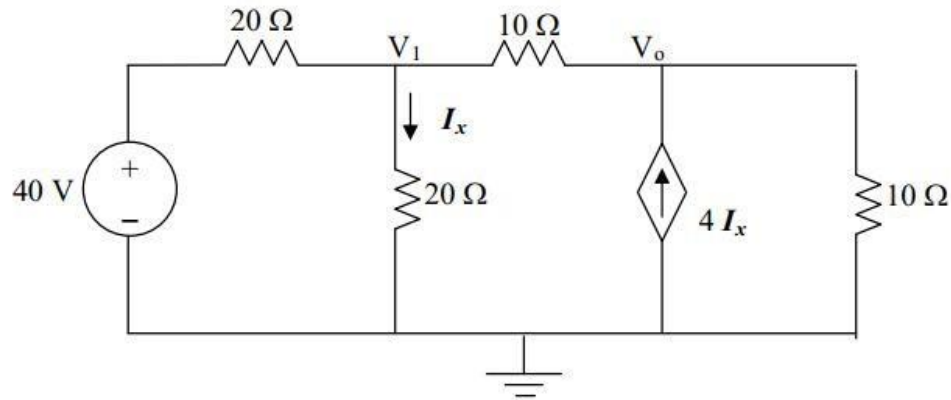

At node 1,

$$\frac{V_1 - 40}{20} + \frac{V_1 - 0}{20} + \frac{V_1 - V_o}{10} = 0 \text{ or}$$

$$(0.05 + 0.05 + 0.1)V_1 - 0.1V_o = 0.2V_1 - 0.1V_o = 2 \quad (1)$$

At node o,

$$\frac{V_o - V_1}{10} - 4I_x + \frac{V_o - 0}{10} = 0 \text{ and } I_x = V_1/20$$

$$-0.1V_1 - 0.2V_1 + 0.2V_o = -0.3V_1 + 0.2V_o = 0 \text{ or} \quad (2)$$


$$V_1 = (2/3)V_o \quad (3)$$

Substituting (3) into (1),

$$0.2(2/3)V_o - 0.1V_o = 0.03333V_o = 2 \text{ or}$$

$$V_o = 60 \text{ V.}$$

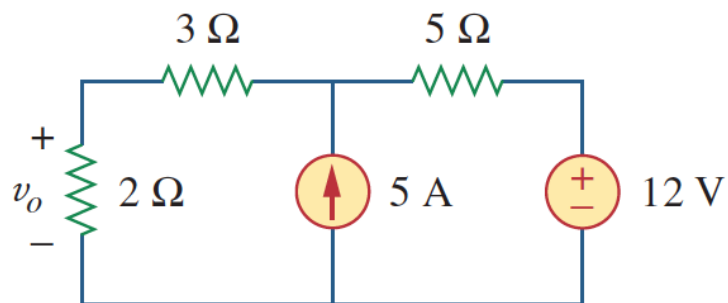Q-4: Using the superposition theorem, find V_o in the circuit of Fig. 4.



Ans:


Since there are 2 sources, let,

$$V_o = V_{o1} + V_{o2}$$

Where V_{01} and V_{02} are the contributions due to the 12V voltage source and the 5A current source, respectively.

When 12 V voltage source is active alone:

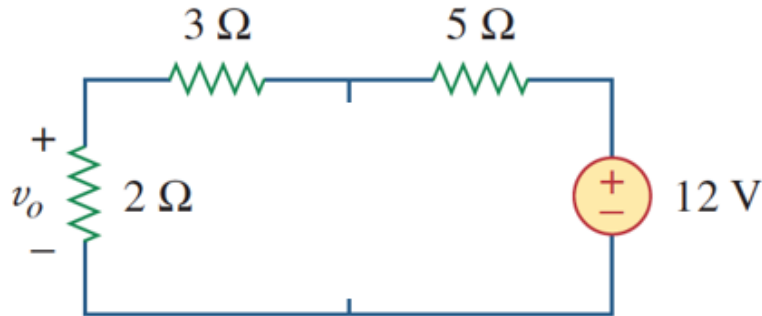To obtain V_{01} , we set the current source to zero by replacing it by open circuit.




Applying Voltage divider rule,

$$V_{01} = \frac{12 \cdot 2}{2 + (5 + 3)} \text{ V}$$
$$= \frac{24}{10} = 2.4 \text{ V}$$

When 5A current source is active alone:

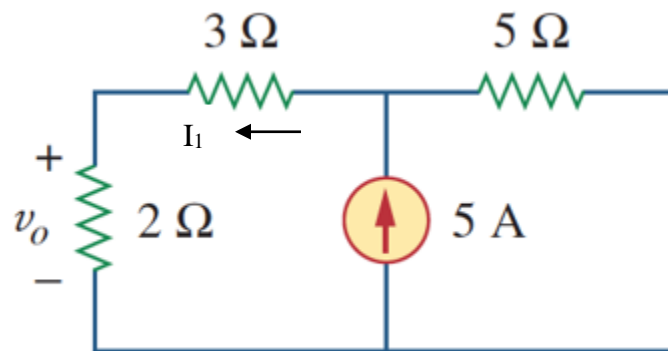To obtain V_{02} , we set the voltage source to zero by replacing it by short circuit.



Let, the current flowing through 2Ω resistor's branch is I_1 . So, applying current divider rule,

$$I_1 = \frac{5 \cdot 5}{5 + (3 + 2)} \text{ A}$$

$$= \frac{25}{10} \text{ A} = 2.5 \text{ A}$$

$$V_{02} = (I_1 * 2\Omega) = (2.5 * 2) \text{ V} = 5 \text{ V}$$

$$\text{So, } V_0 = V_{01} + V_{02}$$

$$= (2.4 + 5) \text{ V}$$

$$= 7.4 \text{ V} \quad (\text{Ans})$$

Q-5: Identify the value of I_1 and I_2 of the following circuit (Fig. 5)

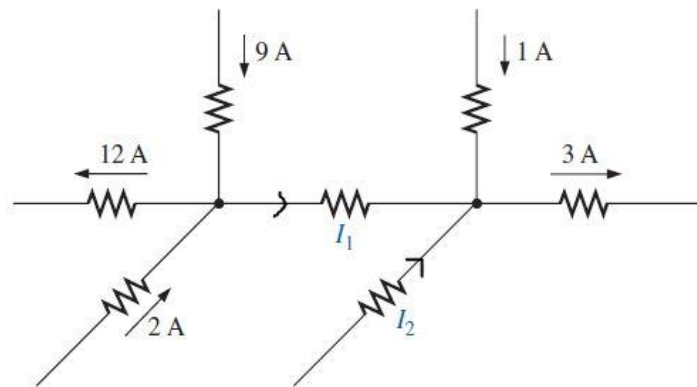


Fig : 5

Ans :

$$12 - 9 - 2 + I_1 = 0$$

$$I_1 = -1 \text{ A}$$

$$3 - 1 + I_2 = 0$$

$$I_2 = -2 \text{ A}$$

Q-6:

6. Read all the statements below and find the correct answers. You may select more than one option.

[a] Ohm's law is applicable for all elements and all conditions.


[b] Current can flow through an open circuit.

[c] Thevenin Theorem cannot be applied in circuits where the resistance of a component changes with voltage or current.

[d] In a circuit if all the resistance have equal value then $R_y < R_{del}$.

Ans: C and D both

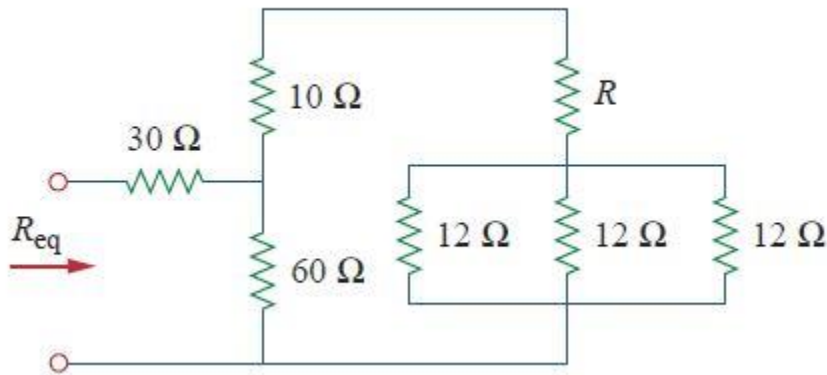Q-7: Suppose R_{eq} is equal to the last two digits of your student ID. Calculate the value of R from the following figure (Fig 6)



Suppose $R_{eq}=50\ \Omega$

Ans:

Let R_0 = combination of three $12\ \Omega$ resistors in parallel

$$\frac{1}{R_0} = \frac{1}{12} + \frac{1}{12} + \frac{1}{12} \longrightarrow R_0 = 4$$

$$R_{eq} = 30 + 60 \parallel (10 + R_0 + R) = 30 + 60 \parallel (14 + R)$$